

İTÜ



# Department of Computer Engineering

## BLG 242E Digital Circuits Laboratory Experiment Report

Experiment : 1 Boolean Algebra

Experiment Date : 01.03.2016

Group Number : 12

Group Members :

ID	Name	Surname
150130032	Baran	Kaya
150130047	Kadir Enes	Karşlıoğlu
150140002	İbrahim	Türkmen
150130133	Eray	Kavuk

Laboratory Assistant : Gökhan Seçinti

# 1 INTRODUCTION

We made 5 different function on experiment. First we tried to understand the device and other equipment's like gates and gate numbers. Then we attached necessary gates on the device and connected gates to the power with cables. Finally, we connect gates to inputs with correct order. After that our circuit run correctly.

## 2 REQUIREMENTS

### 2.1 TRUTH TABLES

Part 1.a)  $F1(a,b) = a + a.b$

A	B	A.B	A + A.B
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

Part 2.b)  $F2(a,b) = (a+b) . (a+b')$

A	B	A+B	A+B'	(A+B).(A+B')
0	0	0	1	0
0	1	1	0	0
1	0	1	1	1
1	1	1	1	1

Part 2) Dual of  $F(a,b) = a+a.b \rightarrow a.(a+b)$

A	B	A+B	A.(A+B)	A+A.B
0	0	0	0	0
0	1	1	0	0
1	0	1	1	1
1	1	1	1	1

Part 3)  $F3(x,y,z) = x+y.z$  complement  $\rightarrow x'.(y'+z')$

X	Y	Z	Y'+Z'	X'.(Y'+Z')
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	0	0

Part 4)  $F4(a,b,c,d) = b.d + b'.d'$

B	D	B.D	B'.D'	B.D + B'.D'
0	0	0	1	1
0	1	0	0	0
1	0	0	0	0
1	1	1	0	1

$$F = A'B'C'D' + A'B'CD' + A'BC'D + A'BCD + AB'C'D' + AB'CD' + ABC'D + ABCD$$

$$F = A'B'D'(C+C') + A'BD(C+C') + AB'D'(C+C') + ABD(C+C')$$


$$F = A'B'D' + A'BD + AB'D' + ABD$$

$$F = BD(A+A') + B'D'(A+A')$$


$$F = BD + B'D'$$

## 2.2 CIRCUITS


Part 1.a)

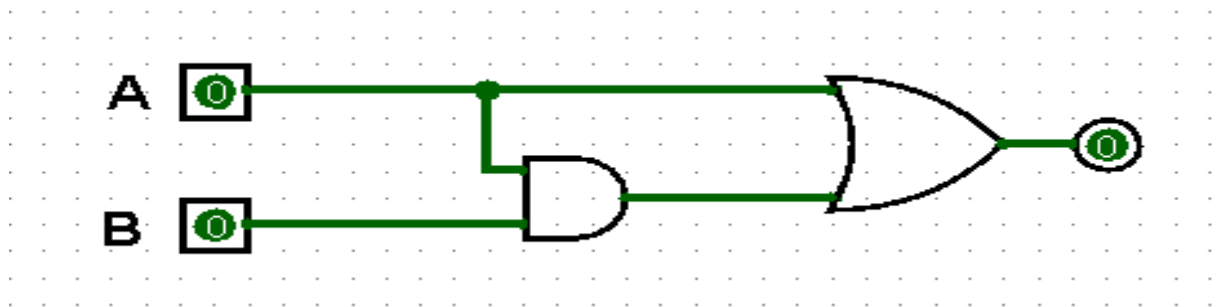


Part 1.b)

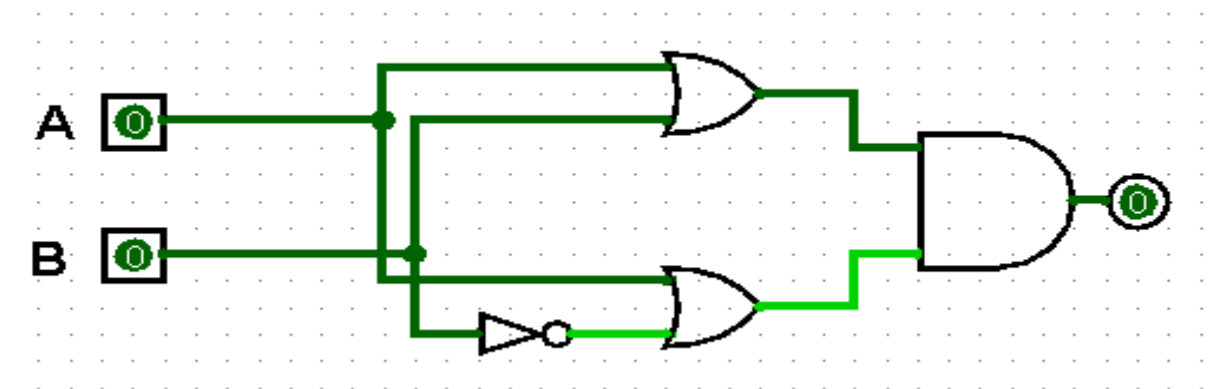


Part 2)

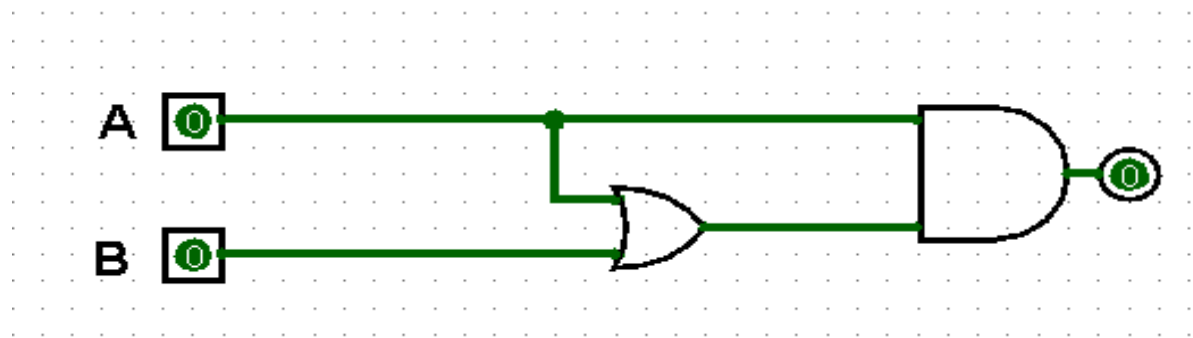

Part 3)

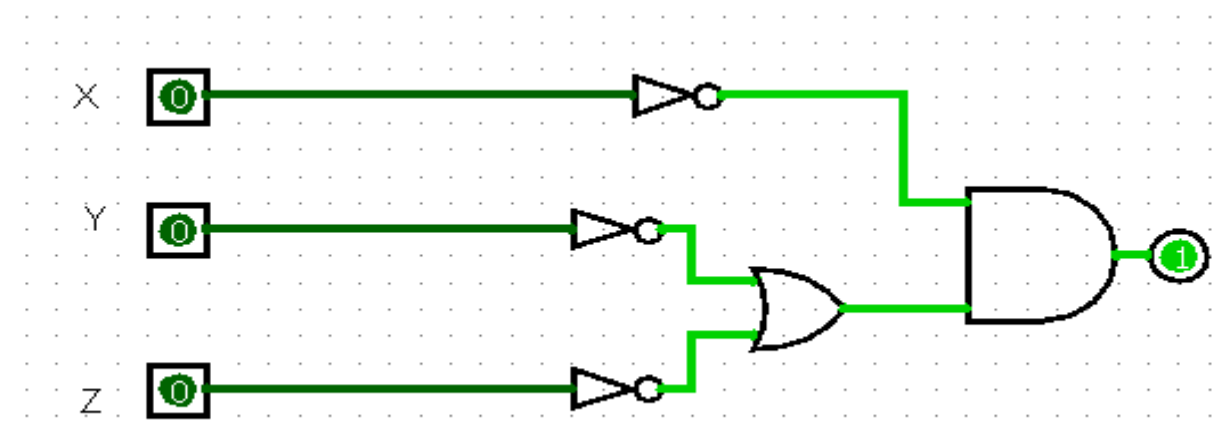

Part 4)

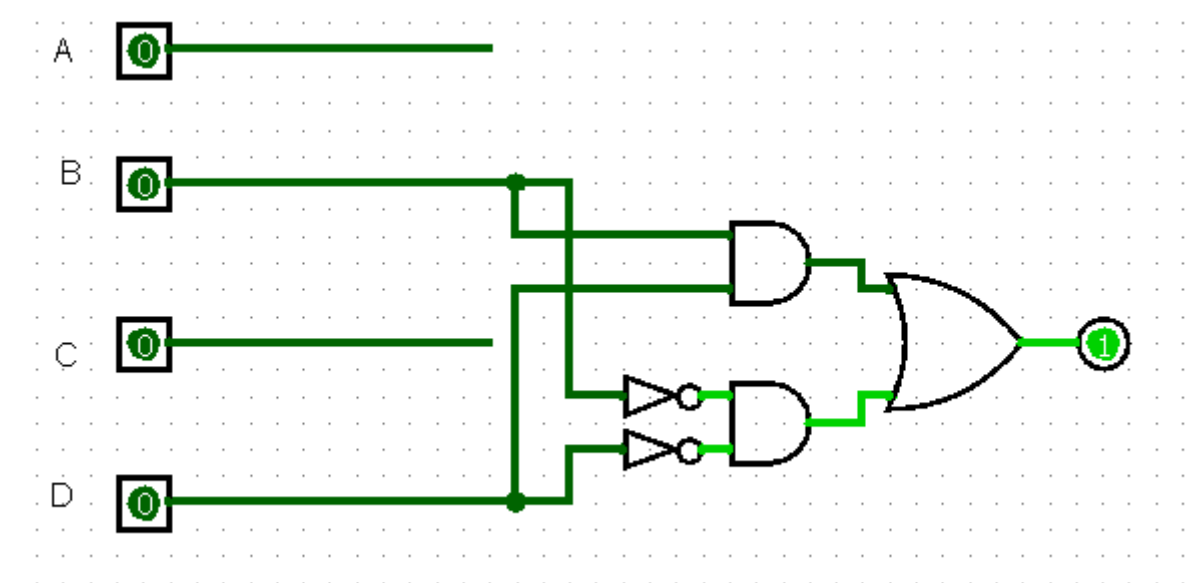

### **3 CONCLUSION**

---

We learnt how to use this device and how to connect power, gates, inputs etc.