

İTÜ



Department of Computer Engineering

BLG 242E Digital Circuits Laboratory Experiment Report

Experiment : 7 Sequential Logic Circuits

Experiment Date : 03.05.2016

Group Number : 12

Group Members :

ID	Name	Surname
150130032	Baran	Kaya
150130133	Eray	Kavuk
Click here to enter text.	Click here to enter text.	Click here to enter text.
Click here to enter text.	Click here to enter text.	Click here to enter text.

Laboratory Assistant : Gökhan Seçinti

1 INTRODUCTION

In this experiment we design 1 bit counter and we used 4 bit counter to build 0-9 counter.

2 REQUIREMENTS

Part 1.

Q1Q0	X = 0	X = 1	Y (Output)
00	10	11	1
01	10	10	0
11	10	10	1
10	00	00	1

Part 2.

We designed 2 bit counter and then built 0-1-2 state table, then we connect the circuit.

Part 3.

We used 4 bit counter and change it to count 0-9. We used reset signal to count 0-9. At 10 (1010) counter reset itself. When S1 and S3 (S3.S1) (AND Gate) are 1 counter reset itself. (S3 S2 S1 S0)

(S1 AND S3 connected to reset signal.)

3 CONCLUSION

We learnt how to use counters and how to implement different counting methods on them with using state diagrams.